
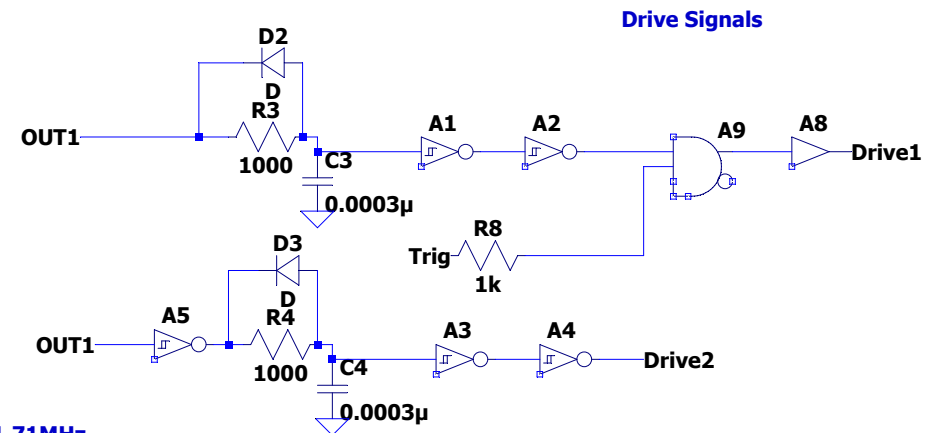


# Tesla Coil Drive Signal Generation

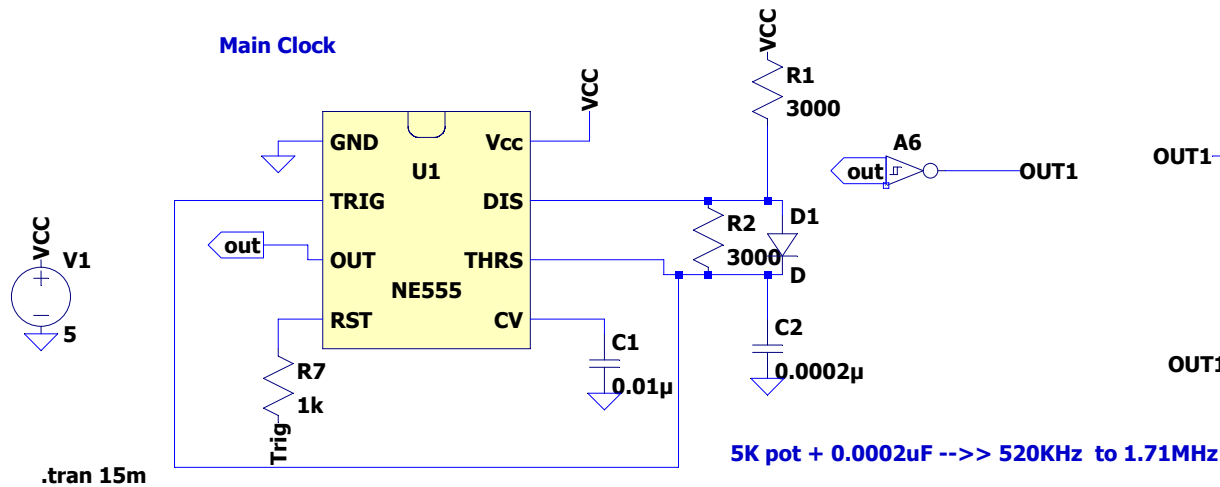

**Note:**

- > Drive1 is complementary of Drive2 with a little "dead time".
- > R1, R2 are potentiometers to tune the frequency.
- > R6 can be used to adjust the duty cycle of the interrupter

