

```
.tran 10m startup
```

by NAMAN TANWAR

1. 2N3904 is used for simulation purpose only.

2. VCC will be much higher than 10v. About 60-240V.

In reality, capacitor banks of 660uF was used in the same fashion.

4. Antenna was shown as another transformer coil for simulation purposes.

